

## Lab 8


### Common Emitter Amplifier

#### Learning outcomes


- 1) Studying the open-loop amplification characteristics of CE circuit
- 2) Studying the effect of load resistance  $R_L$  on amplification characteristics of CE circuit
- 3) Studying the effect of source internal resistance  $R_{sig}$  on amplification characteristics of CE circuit
- 4) Studying the effect of degenerate resistance  $R_E$  on amplification characteristics of CE circuit

#### Experiment 1) Studying the open-loop amplification characteristics of CE circuit

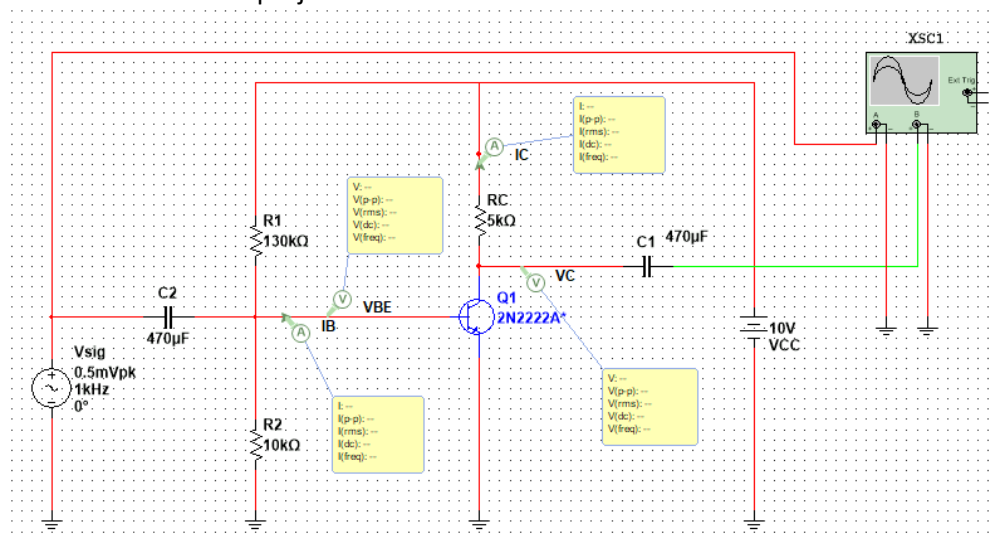- A) Create a new Multisim project and construct the circuit shown



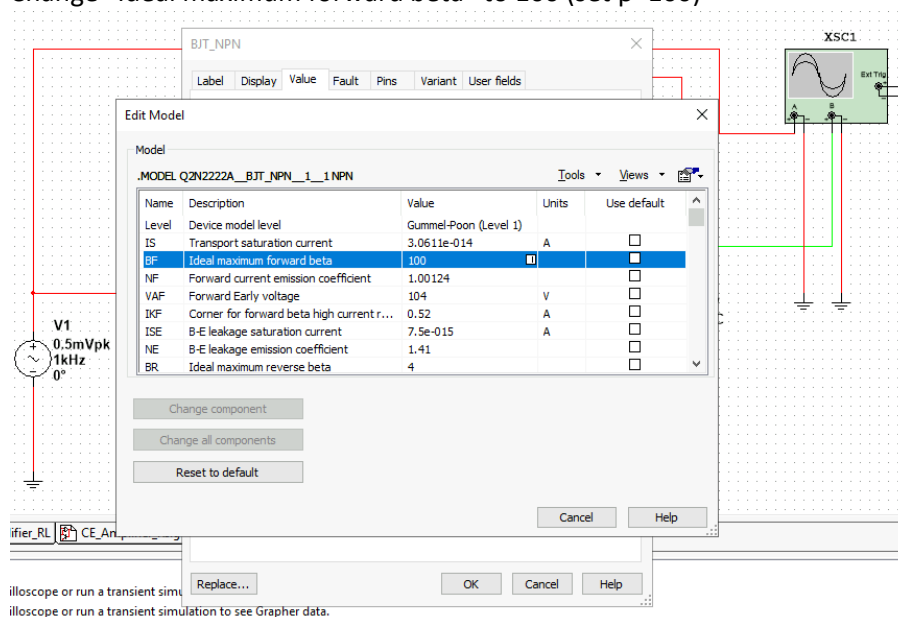
- B) Double click on the BJT transistor then in the “Value” tap click “Edit package”  
 C) Change “Ideal maximum forward beta” to 100 (set  $\beta=100$ )



- D) Run the simulation and record  $I_C$ ,  $V_C$ ,  $V_{BE}$  and calculate  $r_\pi$
- E) Calculate the theoretical values of  $I_C$ ,  $I_B$ ,  $V_C$  (note: use the  $V_{BE}$  measured in (D) not 0.7) then calculate  $r_\pi$
- F) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{\ Measured - Theoretical\ }{Theoretical} \times 100$
$I_B$			
$I_C$			
$V_C$			
$r_\pi$	$V_T/I_B = (25\text{mV}/9.57 \times 10^{-3})$		

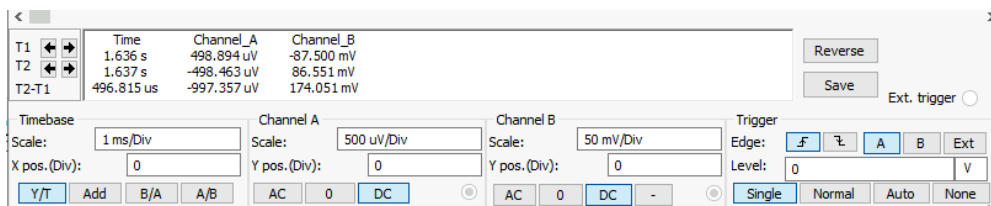- G) Read  $v_{o-pp}$  and  $v_{sig-pp}$  after setting both ChA and ChB as shown below



- H) Take a screenshot of the outputs of the oscilloscope and put it in the following place holder


Put a screenshot of your output ( $v_{o-pp}$  and  $v_{sig-pp}$ ) here and Plz make  $v_{o-pp}$  in green and  $v_{sig-pp}$  in red

- I) Calculate open loop gain  $A_{vo} = v_{o-pp} / v_{sig-pp}$
- J) Calculate the theoretical values of  $A_{vo} = \frac{-\beta R_C}{r_\pi}$
- K) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{\ Measured - Theoretical\ }{Theoretical} \times 100$
$A_{vo}$			

## Experiment 2) Studying the effect of load resistance on the amplification characteristics of CE circuit

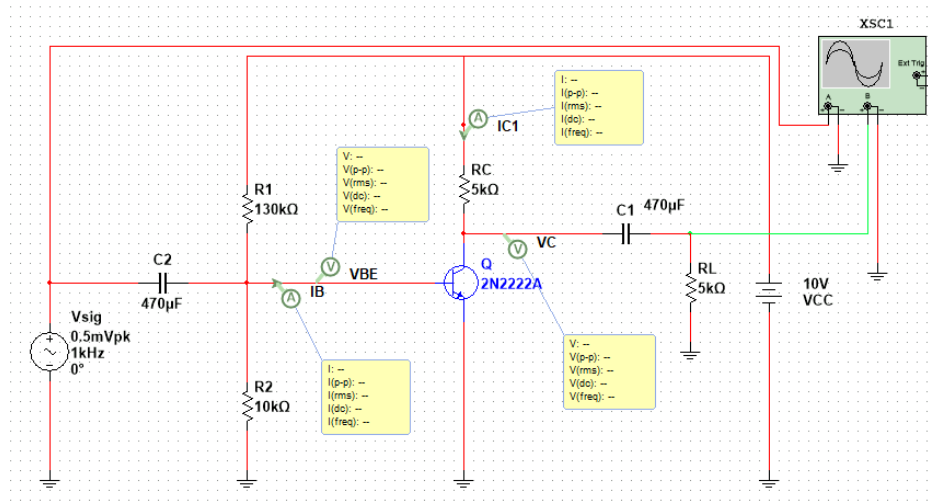- A) Create a new Multisim project and construct the circuit shown (note: copy and paste from exp 1 project but add the new resistance  $R_L$  as a load)




- B) Change “Ideal maximum forward beta” of the transistor to 100 (set  $\beta=100$ ) as explained in exp 1  
 C) Run the simulation and record  $I_C$ ,  $V_C$ ,  $V_{BE}$  and calculate  $r_{\pi}$   
 D) Calculate the theoretical values of  $I_C$ ,  $I_B$ ,  $V_C$  (note: use the  $V_{BE}$  measured in (D) not 0.7) then calculate  $r_{\pi}$   
 E) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{  \text{Measured}-\text{Theoretical}  }{\text{Theoretical}} \times 100$
$I_B$			
$I_C$			
$V_C$			
$r_{\pi}$			

- F) Do you notice any change in  $I_C$ ,  $V_C$ , or  $V_{BE}$  from exp 1? Why or why not? Plz put you answer in the following placeholder

Answer (F) here! (Plz write your answer in red)

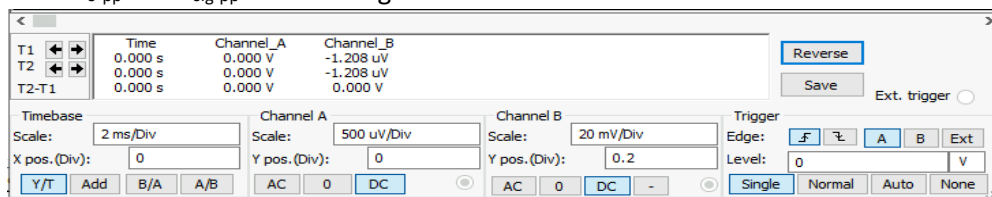- G) Read  $v_{o-pp}$  and  $v_{sig-pp}$  after setting both ChA and ChB as shown below



H) Take a screenshot of the outputs of the oscilloscope and put it in the following place holder

Put a screenshot of your output ( $v_{o-pp}$  and  $v_{sig-pp}$ ) here and Plz make  $v_{o-pp}$  in green and  $v_{sig-pp}$  in red

I) Calculate the voltage gain  $A_v = v_{o-pp} / v_{sig-pp}$

J) Calculate the theoretical values of  $A_v = \frac{-\beta (R_C || R_L)}{r_{\pi}}$

K) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$A_v$			

L) Comparing  $A_v$  to  $A_{vo}$  in exp 1 which is greater and why?

Answer (L) here! (Plz write your answer in red)

M) Repeat the previous procedure at  $R_L = 50\Omega$

N) Based on your measurements and calculations at  $R_L = 50\Omega$  fill the following table


	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$A_v$			

O) Comparing  $A_v$  at  $R_L = 5K\Omega$  to  $A_v$  at  $R_L = 50\Omega$  which is greater and why?

Answer (O) here! (Plz write your answer in red)

### Experiment 3) Studying the effect of internal resistance of source $v_{sig}$ on the amplification characteristics of CE circuit

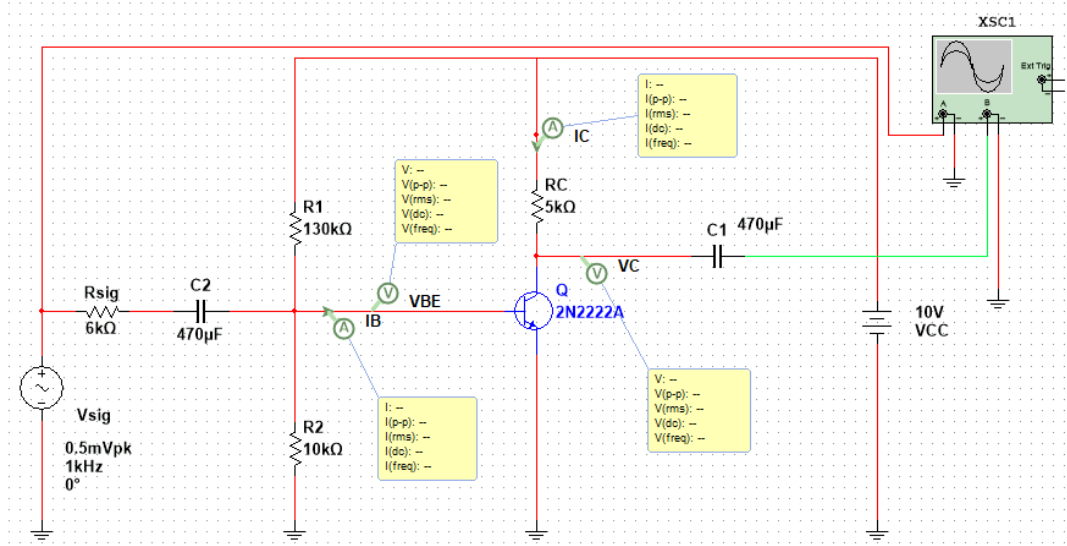- A) Create a new Multisim project and construct the circuit shown (note: copy and paste from exp 1 project but add the new resistance  $R_{sig}$  as an internal resistance of  $V_{sig}$ )




- B) Change “Ideal maximum forward beta” of the transistor to 100 (set  $\beta=100$ ) as explained in exp 1  
 C) Run the simulation and record  $I_C$ ,  $V_C$ ,  $V_{BE}$  and calculate  $r_{\pi}$   
 D) Calculate the theoretical values of  $I_C$ ,  $I_B$ ,  $V_C$  (note: use the  $V_{BE}$  measured in (D) not 0.7) then calculate  $r_{\pi}$   
 E) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$I_B$			
$I_C$			
$V_C$			
$r_{\pi}$			

- F) Do you notice any change in  $I_C$ ,  $V_C$ , or  $V_{BE}$  from exp 1? Why or why not? Plz put you answer in the following placeholder

Answer (F) here! (Plz write your answer in red)

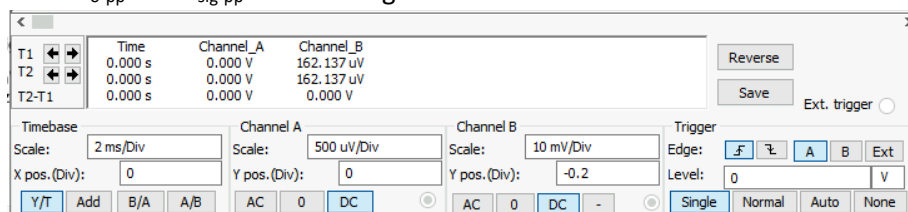- G) Read  $V_{o-pp}$  and  $V_{sig-pp}$  after setting both ChA and ChB as shown below



H) Take a screenshot of the outputs of the oscilloscope and put it in the following place holder

Put a screenshot of your output ( $v_{o-pp}$  and  $v_{sig-pp}$ ) here and Plz make  $v_{o-pp}$  in green and  $v_{sig-pp}$  in red

I) Calculate the overall voltage gain  $G_v = V_{o-pp} / V_{sig-pp}$

J) Calculate the theoretical values of  $G_v = A_v \frac{R_{in}}{R_{in} + R_{sig}}$ , where  $A_v = \frac{-\beta R_C}{r_\pi}$  and  $R_{in} = R_1 || R_2 || r_\pi$

K) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$G_v$			

L) Comparing  $G_v$  to  $A_v$  in exp 1 which is greater and why?

Answer (L) here! (Plz write your answer in red)

M) Repeat the previous procedure at  $R_{sig} = 50\Omega$

N) Based on your measurements and calculations at  $R_{sig} = 50\Omega$  fill the following table


	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$G_v$			

O) Comparing  $A_v$  at  $R_{sig} = 6K\Omega$  to  $A_v$  at  $R_{sig} = 50\Omega$  which is greater and why?

Answer (O) here! (Plz write your answer in red)

#### Experiment 4) Studying the effect of Emitter degenerate resistance on the amplification characteristics of CE circuit

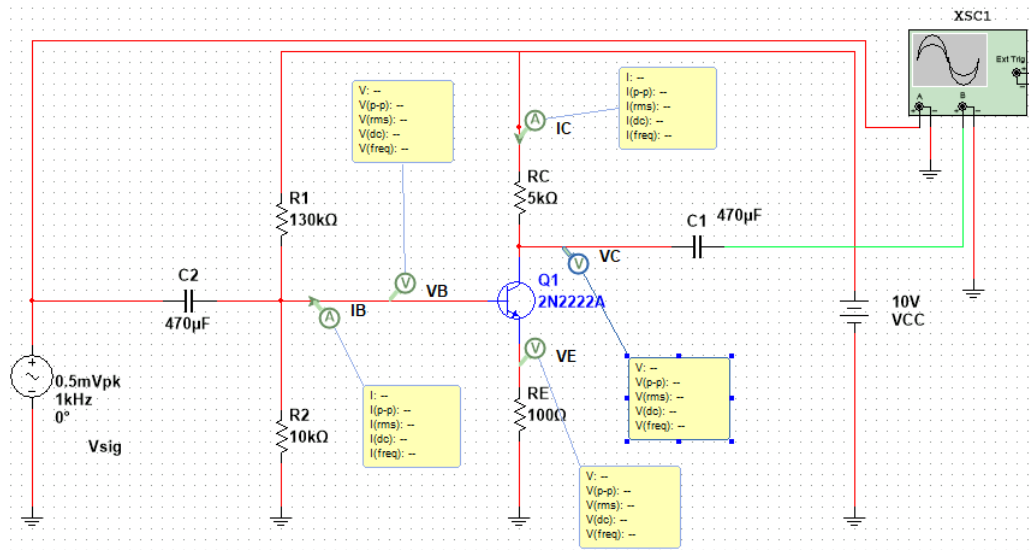- A) Create a new Multisim project and construct the circuit shown (note: copy and paste from exp 1 project but add the new resistance  $R_E$  between Emitter and ground)




- B) Change “Ideal maximum forward beta” of the transistor to 100 (set  $\beta=100$ ) as explained in exp 1  
 C) Run the simulation and record  $I_C$ ,  $V_C$ ,  $V_B$ ,  $V_E$  and calculate  $r_{\pi}$   
 D) Calculate the theoretical values of  $I_C$ ,  $I_B$ ,  $V_C$  (note: use the  $V_{BE}=V_B-V_E$  measured in (D) not 0.7) then calculate  $r_{\pi}$   
 E) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$I_B$			
$I_C$			
$V_C$			
$r_{\pi}$			

- F) Do you notice any change in  $I_C$ ,  $V_C$ , or  $V_{BE}$  from exp 1? Why or why not? Plz put you answer in the following placeholder

Answer G) here! (Plz write your answer in red)

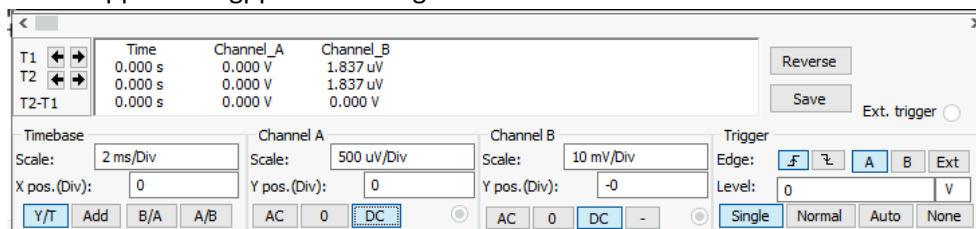- G) Read Vopp and Vsigpp after setting both ChA and ChB as shown below



H) Take a screenshot of the outputs of the oscilloscope and put it in the following place holder

Put a screenshot of your output ( $v_{o-pp}$  and  $v_{sig-pp}$ ) here and Plz make  $v_{o-pp}$  in green and  $v_{sig-pp}$  in red

I) Calculate the overall voltage gain  $A_v = v_{o-pp} / v_{sig-pp}$

J) Calculate the theoretical values of  $A_v = \frac{-\beta R_C}{r_{\pi} + (\beta + 1)R_E}$

K) Based on your measurements and calculations fill the following table

	Measured	Theoretical	Error = $\frac{  Measured - Theoretical  }{Theoretical} \times 100$
$A_v$			

L) Comparing  $A_v$  to  $A_{vo}$  in exp 1 which is greater and why?

Answer (M) here! (Plz write your answer in red)